

Current Knowledge on CKM Front-end Electronics

M. Bowden, K. Bowie, M. Campbell,
P. Cooper, S. Hansen, B. Haynes,
A. Inyakin, M. Kozlovsky,
K. Nelson, Z. Shi, R. Tschirhart,
J. Wu, T. Zimmerman

Feb. 2003

Since 2nd Edition of Proposal


- The front-end electronics, as the data source, need to match the global picture change – software trigger scheme.
- Large amount of new knowledge, test design, simulation, prototype, etc.
- Possible inherits (cost saving): HV (LRS 1440) and crates, PS, racks, etc.

Possible Inherits


- High voltage: LRS 1440 from KTeV.
 - What's the best use of this? FVS? VVS?
 - What about CW development?
 - Work request for experts to study on this.
- Crates, PS, racks, etc: from other experiments.
 - Inventory, quality?
 - Work request for experts to study on this.

CKM FE General Information

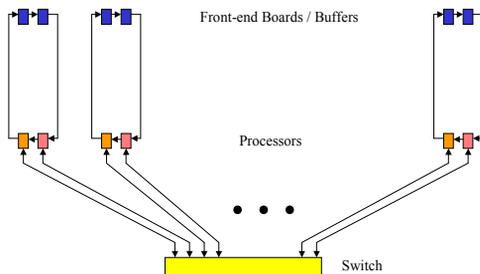- Total channel count: 33K.
 - TDC only channels: 27K.
 - Chambers: UMS, KEAT and DMS.
 - PMT: KRICH, PRICH, BTSM, ETP and CVP.
 - TDC + ADC channels: 6K.
 - PMT: from veto detectors VVS, FVS, BIVS, MVS and HVS.
- Pipeline structure, no DAQ dead time.
- Zero-suppression is needed before sending data through DAQ switch.




Switch-based DAQ Architecture

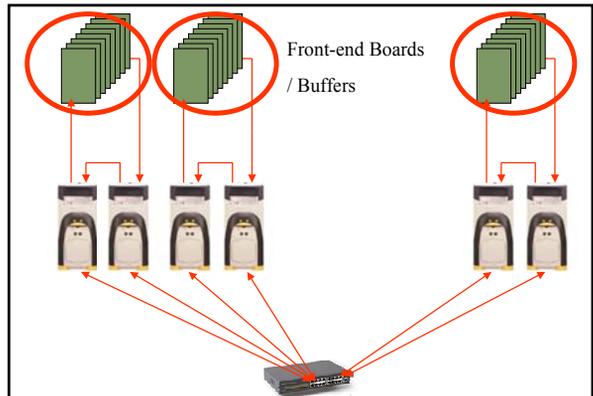


Switch-based DAQ Architecture, Commercial


Details of Front-end Sub-systems

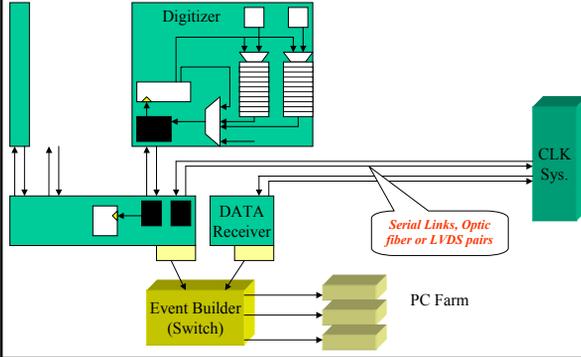


Jlab VVS Prototype PMT Base

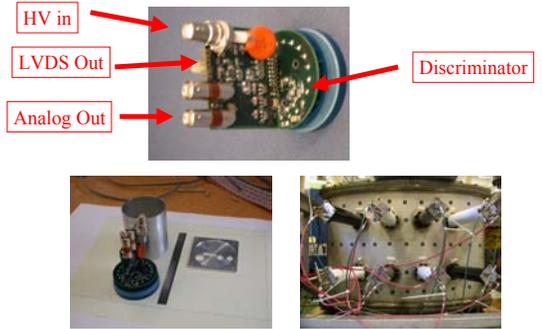

Jlab VVS Prototype PMT Base

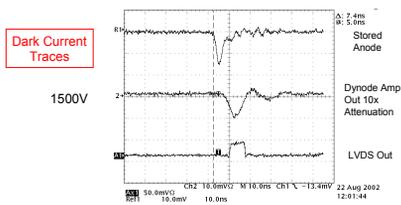


Jlab VVS Prototype PMT Base

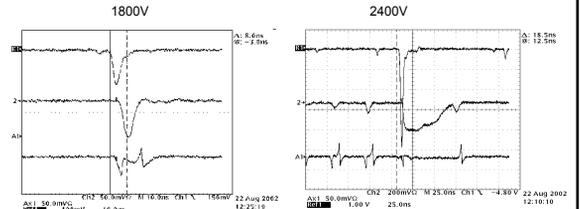

Jlab VVS Prototype PMT Base


- PMT base for VVS prototype were used in Jlab test beam.
- The VVS base with integrated discriminator achieves threshold of 1 MeV.
- Electronics noise is negligible.

CMS QIE Test: FE Card

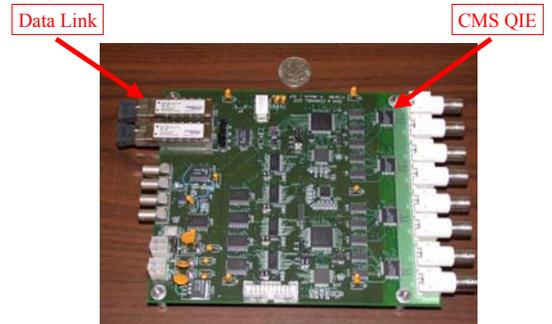

CMS QIE Test: FE Card

Block Diagram

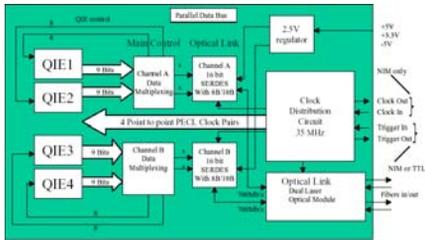


CMS QIE Test: Readout Card

Data Link




- QIE readout card is a modified CoLink card.

CMS QIE Test: Software Interface

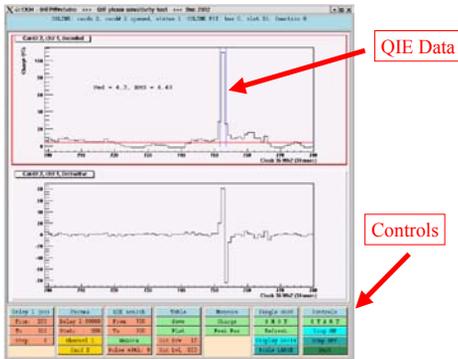


CMS QIE Test: Results

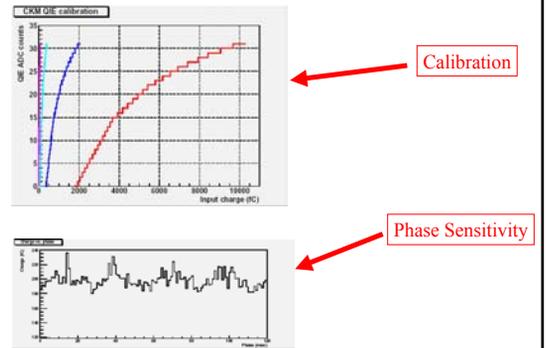


CMS QIE Test: Results

- CMS QIE with 10 m cable has good noise performance with our nominal VVS gain of 1×10^5 and FVS gain 5×10^3 .
- CMS QIE clock phase sensitivity is under control.
- CMS QIE part now runs at 75 MHz, path to 100 MHz and 6-bit mantissa looks clear.


Commercial ADC: The Circuit Board

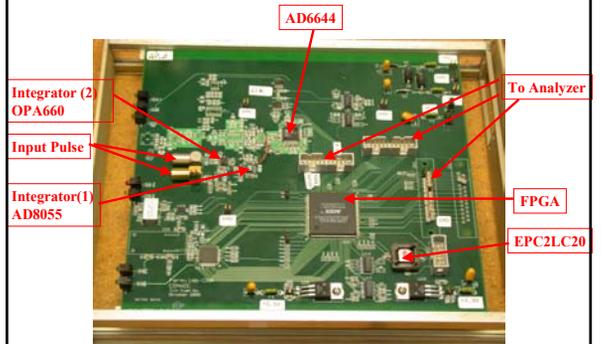

COMADC: 2-phase Integrator

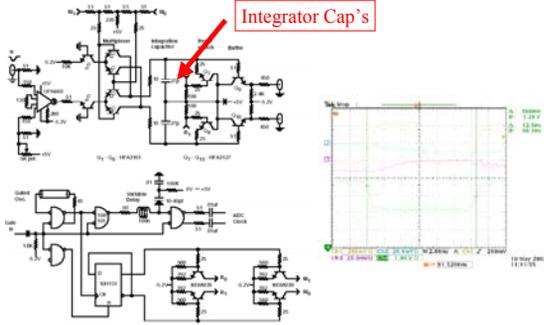


COMADC: Bleeding Integrator

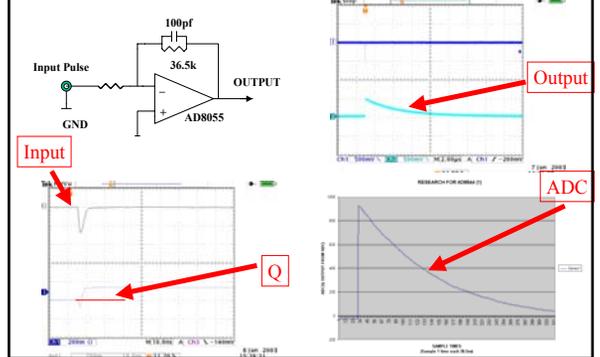


COMADC: Current Findings:

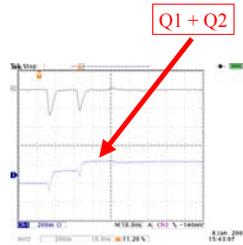- Noise level is under control. (RMS 1.01 to 1.8 LSB or 0.25MeV at 4GeV full scale).
- There is no phase sensitivity issue (for bleeding integrator).
- Linear response provides good multi-pulse detection.




Timing Distribution System (TDS)

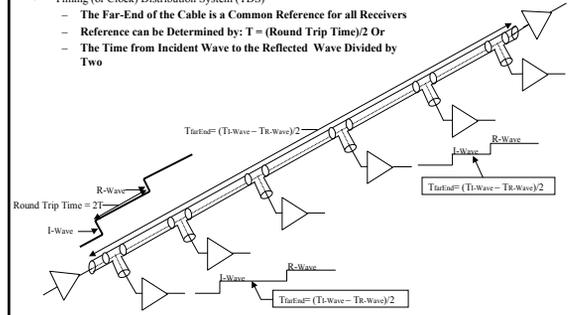- Timing (or Clock) Distribution System (TDS)
 - The Far-End of the Cable is a Common Reference for all Receivers
 - Reference can be Determined by: $T = (\text{Round Trip Time})/2$ Or
 - The Time from Incident Wave to the Reflected Wave Divided by Two



TDS: Block Diagram

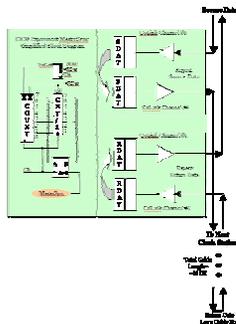- Data patterns are sent through the bi-directional communication links.
- Media delay is sensed by recovered clocks or digital patterns of the data flow.
- Compensated clock is generated with digital method.



TDS: Building Block


Data Link



Timing Distribution System (TDS) & Emergence Service System (ESS)


- Timing distribution system uses digital method to distribute precise timing information over the CKM detector.
- Media delay temperature coefficient is compensated with digital process.
- TDS needs bi-directional communication links -- emergency service system can use the same physical system, just add firm-wares.

TDC, DESER Based:

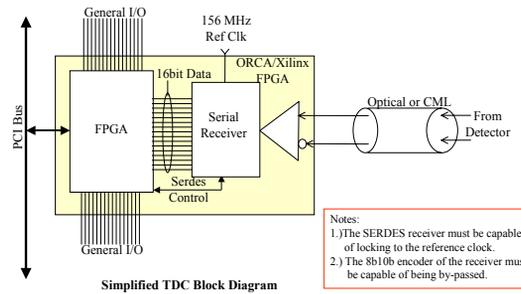


TDC, DESER Based: Simulation


- TDC w/ 400ps Resolution
 - Input Pulse Width = $7FFF\ FC00\ 0000 > 21\text{bits} \times 6.4\text{ns}/16 = 21 \times 400\text{ps} = 8.4\text{ns}$
 - Reference Counter Time = $T_{\text{Ref}} = 105.6\text{ns}$
 - $T_{\text{Ref}} \text{ Offset} = \# \text{ of } 0 \text{ bits from } T_{\text{Ref}} \times 400\text{ps} = 1 \times 400\text{ps} = 400\text{ps}$
 - Input Prop. Delay = $28.800075\text{ns} + T_{\text{Ref}} \text{ Offset} = 28.800075\text{ns} + 400\text{ps} = 29.200075\text{ns}$

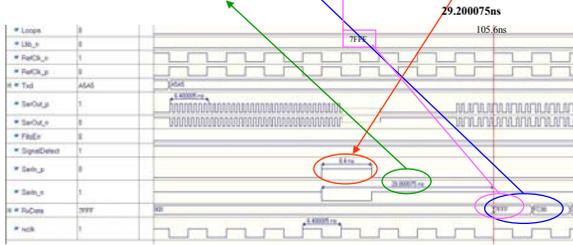


TDC, Chain Delay Based:

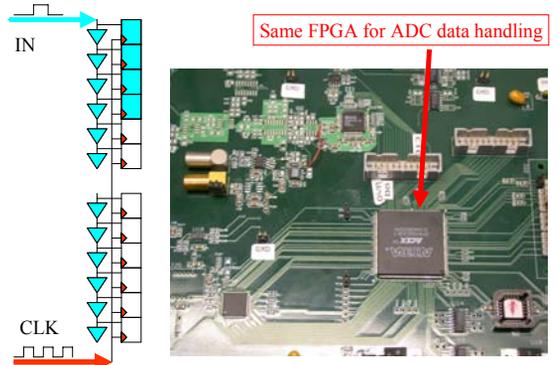


TDC, Chain Delay Based: Test

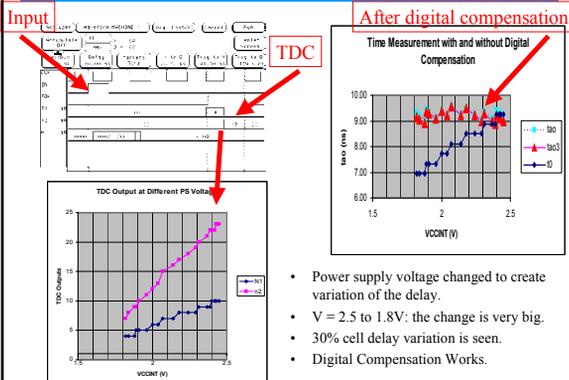

UMS Pre-amplifier

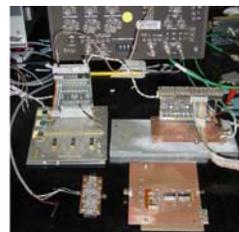

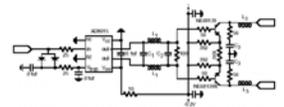
- Both UPENN-ASDQ and commercial-part-based ASD are tested.
- Left: test setup.
- Bottom: COM-ASD circuit schematics.




UMS Pre-amplifier

- Measured:
 - Equivalent noise charge (ENC) at input.
 - T_r
- COM-ASD works as good as UPENN-ASDQ.


DMS Pre-amplifier: Schematics

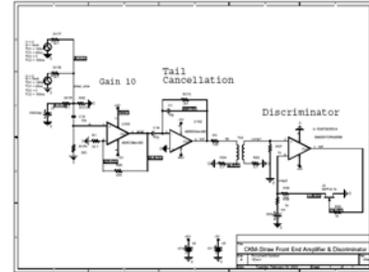


DMS Pre-amplifier: Simulation

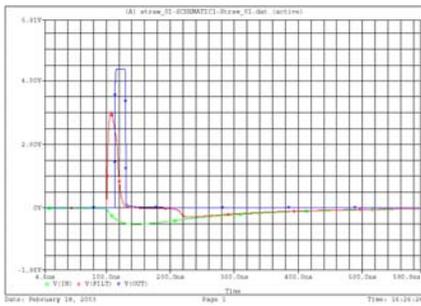

RICH PMT Base: Structure

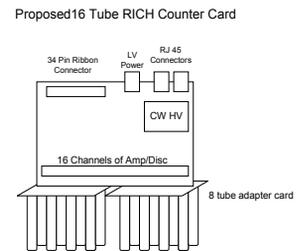



RICH PMT Base: Adapter Card

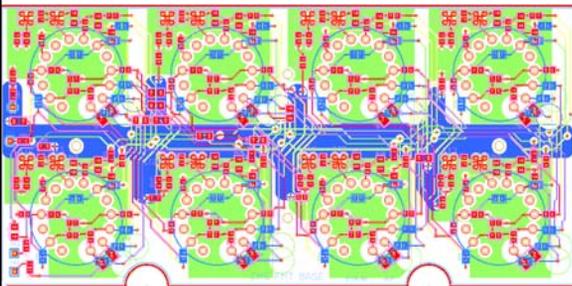

Data Structure Study

- Data sparsification is necessary in FE hardware.
- A scheme of possible data structure is provided for software trigger simulation based current knowledge on hardware.

Data Structure		1 1 0 1		Check sum of past centenary			
Centenary 255	0	E	D	TS[7:0]	Time (1ns/bin)		
	1	1	0	0	TS[9:6]	Ch. #	
	1	1	0	0	Centenary ID = TS[15:8]		
	1	1	0	1	Check sum of past centenary		
Centenary 0	0	E	D	TS[7:0]	Time (1ns/bin)		
	1	1	0	0	TS[9:6]	Ch. #	
	1	1	0	0	Centenary ID = TS[15:8]		
	1	1	0	1	Check sum of past centenary		
Centenary ID word: Inserted while forming Millenary		1	1	1	1	Millenary Check Sum [11:0]	
Millenary Header		1	1	1	1	Millenary Word Count [23:12]	
		1	1	1	1	Millenary Word Count [11:0]	
		1	1	1	1	Unified Channel Number [23:12]	
		1	1	1	1	Unified Channel Number [11:0]	
		1	1	1	1	Reset ID [3:0]	Millenary ID [31:24]
		1	1	1	1	Millenary ID [23:12]	
		1	1	1	0	Millenary ID [11:0]	

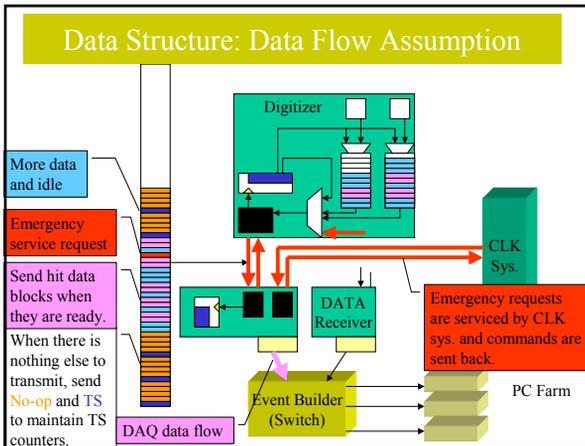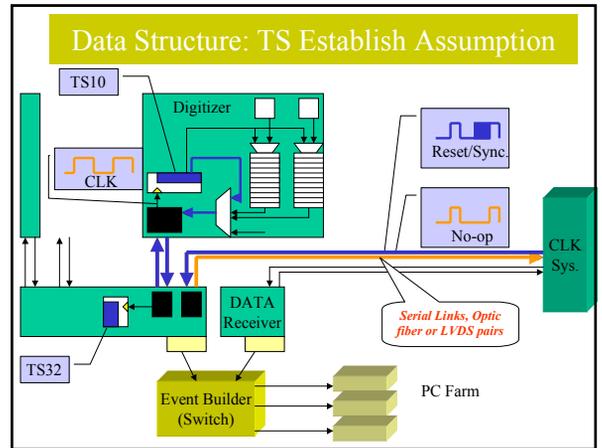

The End

Thanks